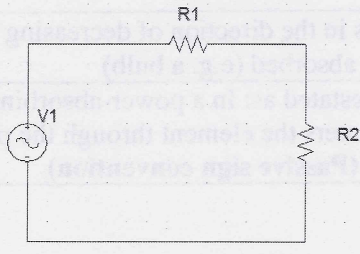
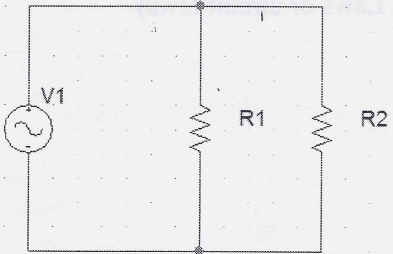


Resistance Properties

Two resistors in series:

	$R_S = R_1 + R_2$
---	-------------------

Two resistors in parallel:

	$\frac{1}{R_P} = \frac{1}{R_1} + \frac{1}{R_2}$
--	---